

EE230: Analog Circuits Lab

Square Root Amplifier Implementation

Lab No. 5

Anupam Rawat, 22b3982

February 2, 2024

1 Aim of the experiment

Construct a square root amplifier and fine tune it to utmost precision

2 Design

The current through the diode in forward bias is given by the following equation

$$I_D = I_S * (e^{V_D/nV_T} - 1) \quad (1)$$

Rearranging the terms we get

$$V_D = n \cdot V_T * (\ln(I_D) - \ln(I_S)) \quad (2)$$

The output of Block-1 is given by V_{out1} :

$$V_{out1} = -V_D = n \cdot V_T * (\ln(I_S R) - \ln(V_{in})) \quad (3)$$

The output of Block-2 is given by V_{out2} :

$$V_{out2} = -n \cdot V_T \cdot \ln(I_S R) + (\ln(V_{in}))V_T \cdot n + 2V_{b1} \quad (4)$$

We can remove the offset terms which don't include V_{in} by choosing:

$$V_{b1} = \frac{n \cdot V_T \cdot \ln(I_S \cdot R)}{2} \quad (5)$$

$$V_{out2} = n \cdot V_T \cdot \ln(V_{in}) \quad (6)$$

The output of Block-3 can be given by:

$$V_{out3} = -\frac{R_{22}}{R_{21}} \cdot V_{out2} = -\frac{R_{22}}{R_{21}} \cdot V_T \cdot \ln(V_{in}) = \ln(V_{in}^{-\frac{R_{22}}{R_{21}}} n^V T) \quad (7)$$

For Block-4, $V_x = V_{b2}$ (virtual ground) and:

$$V_{out} = R_3 \cdot I_{D2} + V_{b2} = R_3 \cdot T_{S2} \cdot e^{\frac{V_{b2}}{n_2 \cdot V_T}} V_{in}^{\frac{n_1}{n_2} \frac{R_{22}}{R_{21}}} + V_{b2} \quad (8)$$

We can simplify the circuit as:

$$V_{R3} = V_{out} - V_x = \beta_1 \cdot V_{in}^{\beta_2} \quad (9)$$

For square root amplifier, we can choose $\beta_1 = 1$ and $\beta_2 = \frac{1}{2}$

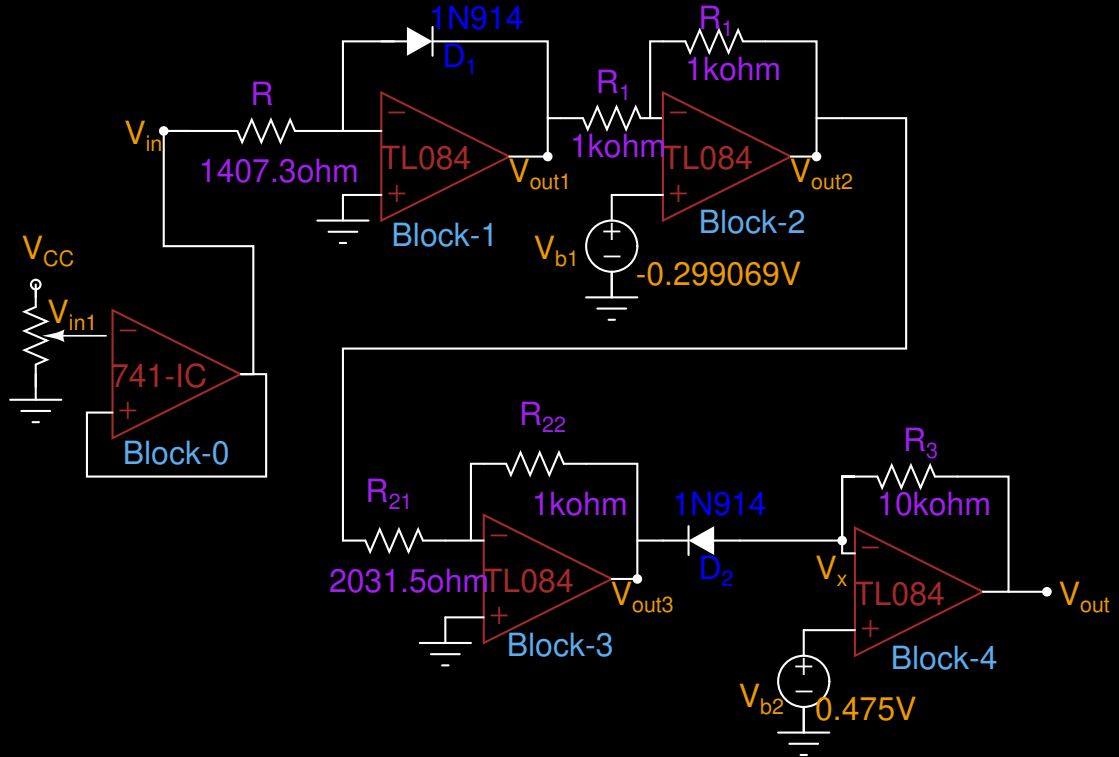


Figure 1: Circuit Diagram

3 Experimental results

What is the purpose of Block - 0:

Block 0 is a voltage buffer. It provides very high input impedance and about zero output impedance.

What if V_{in} is directly connected to V_{in1} :

If V_{in} is directly connected to V_{in1} ; loading effect will be caused and current flowing through the potentiometer in block 0 could cause unnecessary losses in current.

Derive both V_{b1} and V_{b2} DC voltages using multi turn potentiometer:

at $V_{in} = 1V$, $V_{out2} = 0V$.

Adjusting V_{b1} to get 0V output, we get $V_{b1} = -0.24V$ and on fine tuning we get $V_{b2} = 0.44V$.

Why V_{b2} potentiometer is coarse measurement whereas $R3$ is a fine one:

As it can be seen from the **equation (9)** that V_{R3} is directly proportional to $\exp(\frac{V_{b2}}{n_2 \cdot V_T})$. Now since, $1 / (n_2 \cdot V_T) \gg 1$, a slight change in the value of V_{b2} leads to a huge change in the value of V_{R3} . And it can also be seen from the **equation (9)** that V_{R3} is directly proportional to R_3 . And since we know that after the input value crosses the 1 mark, the exponential value increases very rapidly as compared to the linear dependence. Hence, the V_{b2} is a coarse adjustment while R_3 is a fine adjustment.


GO TO NEXT PAGE —————->

Sweep V_{in} from 1V to 15V in uniform steps of 1V. Tabulate your readings:


These are simulation results.

V_{in} (in Volts)	V_{R3} (in Volts)	V_{in} (in Volts)	V_{R3} (in Volts)
1	0.95388	2	1.357
3	1.68	4	1.95
5	2.184	6	2.407
7	2.60	8	2.813
9	3.0003	10	3.184
11	3.360	12	3.532
13	3.698	14	3.862
15	4.021	16	4.179

Plot V_{out} v/s V_{in} :

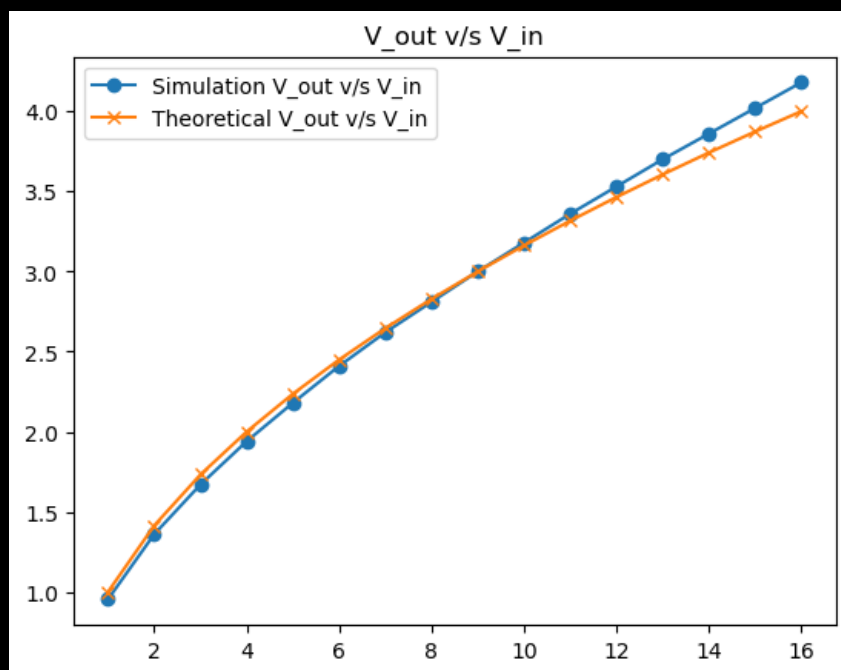

Plot $\ln(V_{out})$ v/s $\ln(V_{in})$:

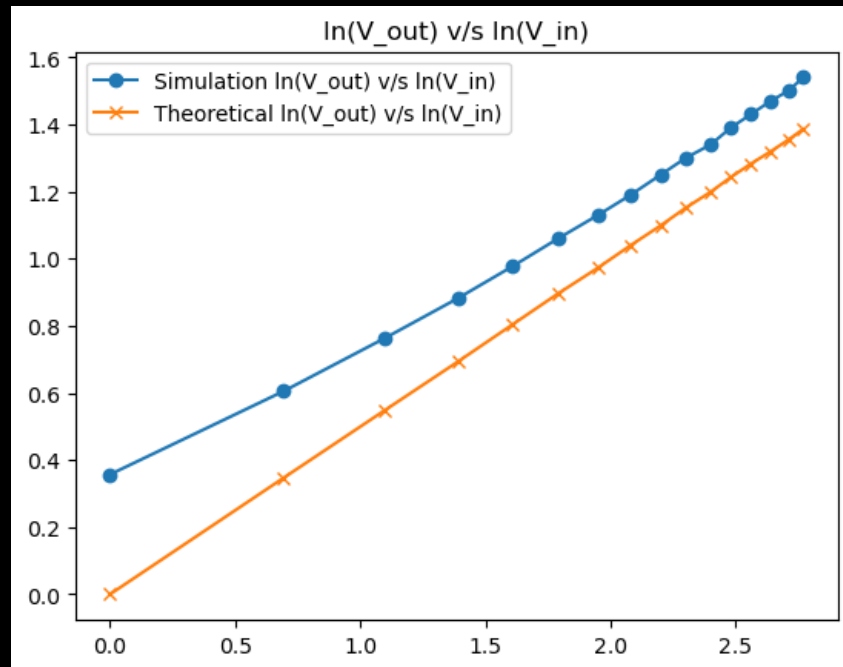

What should be the expected slope of the above plot:

The expected slope of the above plot which is $\ln(V_{out})$ v/s $\ln(V_{in})$ should be 0.5

What happens if the polarity of the diode D_2 is reversed:

Reversing D_2 's polarity may lead to non-linear behavior, impacting amplifier effectiveness. Maintaining correct diode orientation is crucial

4 Experiment completion status

The observation values could not be taken during the experiment. The circuit connections was completely correct and was also verified by two TAs and an RA.

We faced saturation after block-1. The output of block-1 was 13.47V which ideally should have been around -0.589V and hence the output of block-2 was 14.57V which ideally should have been 0V.

The TAs and RAs also couldn't help much with this. We changed the IC, diodes several times. We also explored the possibility of having a faulty LM741 but that was also not the case. We also didn't keep the circuit in ON state for too long and were also repeatedly checking for any blown up potentiometers, but that was also not the case. We verified other values before block-1, which were totally correct. We concluded that we were facing some issues after block-1. And this problem was faced by a lot of groups in the lab.

We along with TAs, RAs tried debugging for 1.5 hours, but it didn't help much and in the end, we couldn't take any observations.