

EE 230: Analog Circuits Lab  
Lab No. 6  
Non Idealities in the Op-Amp

Anupam Rawat, 22b3982

February 9th, 2024

## Section - A (Offset voltage and Bias currents)

### 1. Measurement of $V_{os}$ - offset voltage:

#### 1.1 Aim of the experiment

Measure the offset voltage  $V_{os}$  and compare it with the device specifications as per the dataset.

#### 1.2 Design

Equations regarding the circuit:


$$V_o = V_{os} \cdot \left(1 + \frac{R_2}{R_1}\right) + R_2 \cdot I_{B-} \quad (1)$$

$$V_o \approx V_{os} \cdot \left(\frac{R_2}{R_1}\right) \quad (2)$$

$$V_{os} \approx \frac{V_o}{\frac{R_2}{R_1}} \quad (3)$$

We can use the approximation because the ratio of  $R_2/R_1$  is  $\gg 1$

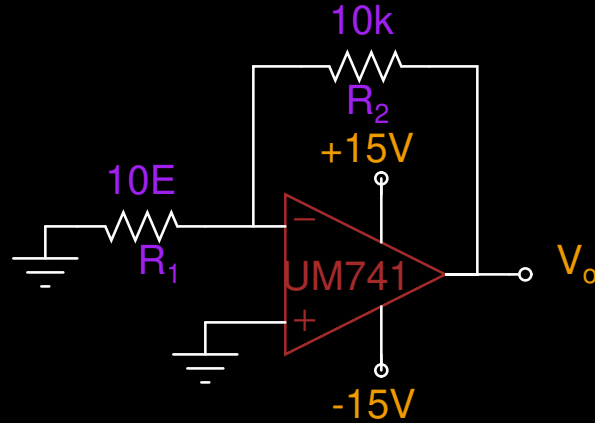Below is the circuit diagram for the experiment:



### 1.3 Experimental results

Measured values of Resistances and output voltage  $V_o$ :

The value of the resistances are  $R_1 = 10.3\Omega$  and that of  $R_2 = 9.97\Omega$ . The output voltage  $V_o = 1.24V$ .

What is measured  $V_{os}$   

$$V_{os} = \frac{1.24V}{\frac{9.97k\Omega}{10.3\Omega}} = 1.28 \text{ mV}.$$

From datasheet  $V_{os}$  typical is 1mV.

### 1.4 Experiment completion status

The experiment was completed during lab hours and the hand written report for the same was also submitted during lab hours.

## 2. Measurement of Bias Current $I_{B-}$


### 2.1 Aim of the experiment

The experiment required measurement of  $I_{B-}$  and comparison as per the dataset.
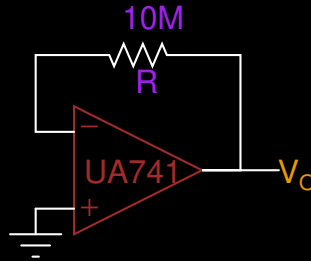
### 2.2 Design

$$V_- = V_+ = V_{os} \quad (4)$$

$$V_o = V_- + I_{B-} \cdot R = V_{os} + I_{B-} \cdot R \quad (5)$$



### 2.3 Experimental results

#### Measured values of Resistances and output voltage $V_o$

The measured value of  $R = 9.66\text{M}\Omega$  and the measured value of  $V_o$  is 365mV.

#### What is the measured value of $I_{B-}$ and compare with the dataset

The value of  $I_{B-} = \frac{V_o}{R} = 37.01\text{nA}$ .

From datasheet, the typical value of  $I_B = 10\text{nA}$  and the maximum value of  $I_B = 100\text{nA}$ .

### 2.4 Experiment completion status

The experiment was completed during lab hours and the hand written report for the same was also submitted during lab hours.

### 3. Measurement of Bias Current $I_{B+}$ :


#### 3.1 Aim of the experiment

The experiment required measurement of  $I_{B+}$  and comparison as per the dataset.

#### 3.2 Design

$$V_+ = I_{B-} \cdot R + V_{os} = V_o = V_+ = V_- \quad (6)$$

$$I_{B+} = \frac{V_o}{R} \quad (7)$$

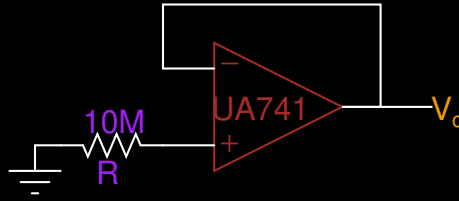

#### 3.3 Experimental results

##### Measured values of Resistances and output voltage $V_o$

The measured value of  $R = 9.66\text{M}\Omega$  and the measured value of  $V_o$  is  $-378\text{mV}$ .

##### What is the measured value of $I_{B+}$ and compare with the dataset

The value of  $I_{B+} = \frac{V_o}{R} = -38.33\text{nA}$ .

From datasheet, the typical value of  $I_B = 10\text{nA}$   
and the maximum value of  $I_B = 100\text{nA}$ .

#### 3.4 Experiment completion status

The experiment was completed during lab hours and the hand written report for the same was also submitted during lab hours.

## Section - B (Open Loop Gain ( $A_{OL}$ ))

### 2. Measurement of Open Loop Gain

#### 2.1 Aim of the experiment


Calculate the value of open loop gain in the UA741 IC Op-Amp.

#### 2.2 Design

$$V_- = -\frac{V_o}{A_{OL}} \quad (8)$$

$$V_R = V_- \cdot \left(\frac{R_1 + R_2}{R_2}\right) \quad (9)$$

$$|A_{OL}| = \frac{|V_o|}{|V_R|} \cdot \left(\frac{R_1 + R_2}{R_2}\right) \quad (10)$$

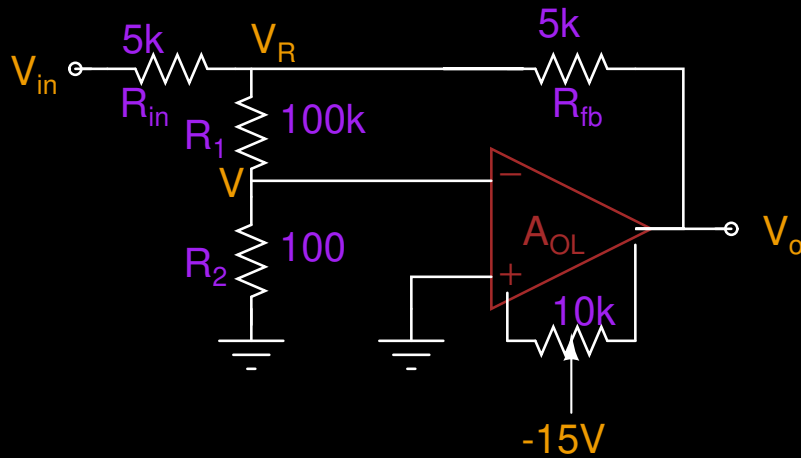

#### 2.3 Experimental results

What are the actual values of Resistances:

The value of  $R_{in} = 5.02\text{k}\Omega$ ,  $R_{fb} = 5.05\text{k}\Omega$ ,  $R_1 = 98.0\text{k}\Omega$  and  $R_2 = 100.6\Omega$

$f(Hz)$	$V_o$	$V_R$	$A_{OL}$
10k	80mV	720mV	108.35
1k	560mV	680mV	803.07
500	936mV	592mV	1541.79
100	1.50V	188mV	7780.49
20	1.54V	42mV	35755.68
10	1.54V	26mV	57759.18
9	1.54V	24mV	62572.45
8	1.54V	21.6mV	69524.94
7	1.54V	20.8mV	72198.98
6	1.54V	19.2mV	78215.56
5	1.54V	17.6mV	85326.06
4	1.54V	16mV	93858.67
3	1.54V	13.5mV	111239.90
2	1.54V	13.7mV	109676.00
1	1.54V	11.4mV	131731.50

Values of  $V_o, V_R$  and  $A_{OL}$  at various frequencies:

Roll off slope of  $A_{OL}$

Roll off slope of  $A_{OL} = 37.84 / 2 = - 18.57$

What is the 3dB frequency of the OpAmp:

The 3dB frequency of the OpAmp is  $\approx 4\text{Hz}$ .


What is the measured open loop gain of the OpAmp:

Calculated open loop gain  $A_{OL} = 1.31 \times 10^5$

As per the dataset, the typical value of the dataset is  $2 \times 10^5$ .

What is pole frequency of the OpAmp:

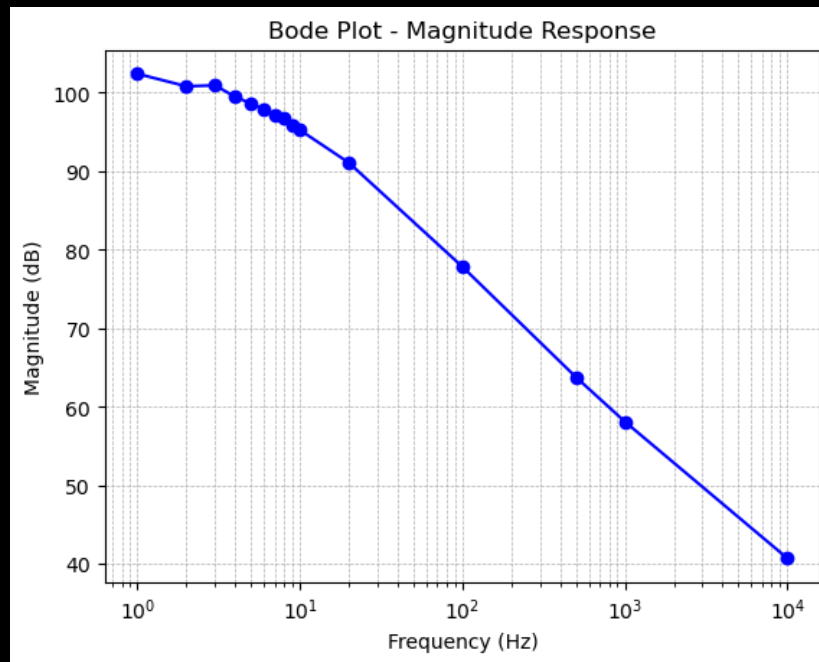Magnitude frequency response of the open loop gain has 1 pole, and the pole frequency is  $\approx 100\text{Hz}$ .



## 2.4 Simulation

## 2.5 Experiment completion status

The experiment was completed during lab hours and the hand written report for the same was also submitted during lab hours.

Parameter	Experimental Values	Datasheet value
$V_{OS}$	1.28mV	1mV
$I_{B-}$	37.0nA	10nA
$I_{B+}$	38.35nA	10nA
$A_{OL}$	$1.31 \times 10^5$	$2 \times 10^5$

## Conclusion of The Experiment

The experimentally calculated values of the experiment agree well with the values in the dataset of UA741.