

EE230: Analog Circuits Lab

Square Root Amplifier

Lab No. 4

Anupam Rawat, 22b3982

January 25, 2024

1 Aim of the experiment

Construct a square root amplifier and fine tune it to utmost precision

2 Design

The current through the diode in forward bias is given by the following equation

$$I_D = I_S * (e^{V_D/nV_T} - 1) \quad (1)$$

Rearranging the terms we get

$$V_D = n \cdot V_T * (\ln(I_D) - \ln(I_S)) \quad (2)$$

The output of Block-1 is given by V_{out1} :

$$V_{out1} = -V_D = n \cdot V_T * (\ln(I_S R) - \ln(V_{in})) \quad (3)$$

The output of Block-2 is given by V_{out2} :

$$V_{out2} = -n \cdot V_T \cdot \ln(I_S R) + (\ln(V_{in}))V_T \cdot n + 2V_{b1} \quad (4)$$

We can remove the offset terms which don't include V_{in} by choosing:

$$V_{b1} = \frac{n \cdot V_T \cdot \ln(I_S \cdot R)}{2} \quad (5)$$

$$V_{out2} = n \cdot V_T \cdot \ln(V_{in}) \quad (6)$$

The output of Block-3 can be given by:

$$V_{out3} = -\frac{R_{22}}{R_{21}} \cdot V_{out2} = -\frac{R_{22}}{R_{21}} \cdot V_T \cdot \ln(V_{in}) = \ln(V_{in}^{-\frac{R_{22}}{R_{21}}} n V_T) \quad (7)$$

For Block-4, $V_x = V_{b2}$ (virtual ground) and:

$$V_{out} = R_3 \cdot I_{D2} + V_{b2} = R_3 \cdot T_{S2} \cdot e^{\frac{V_{b2}}{n_2 \cdot V_T}} V_{in}^{\frac{n_1}{n_2} \frac{R_{22}}{R_{21}}} + V_{b2} \quad (8)$$

We can simplify the circuit as:

$$V_{R3} = V_{out} - V_x = \beta_1 \cdot V_{in}^{\beta_2} \quad (9)$$

For square root amplifier, we can choose $\beta_1 = 1$ and $\beta_2 = \frac{1}{2}$



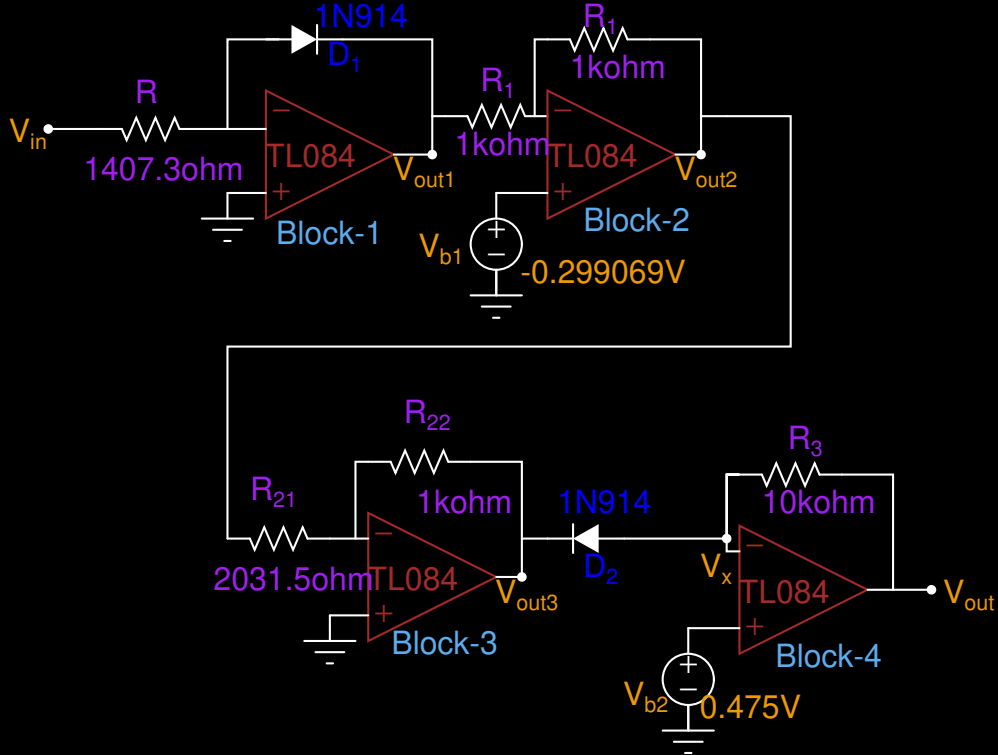
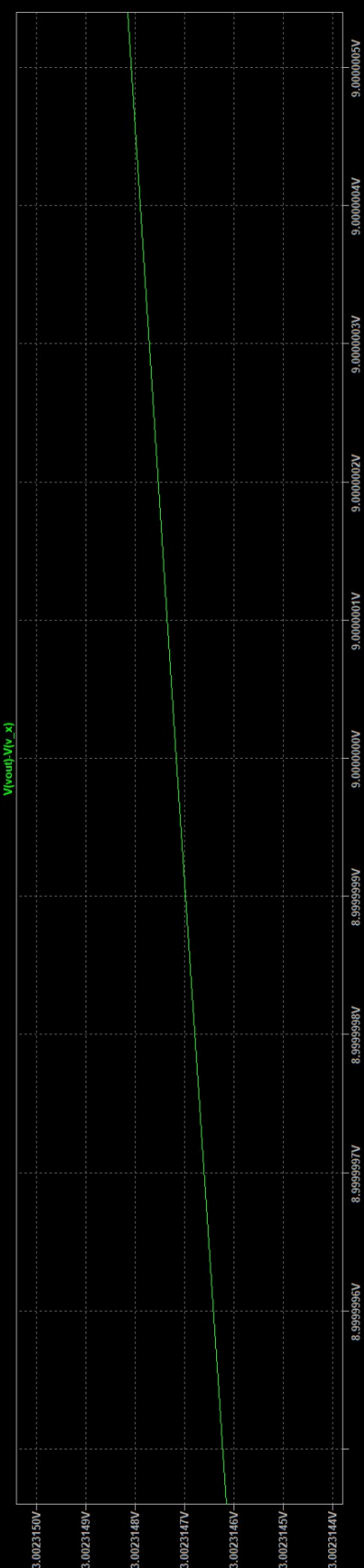


Figure 1: Circuit Diagram

3 Simulation Results

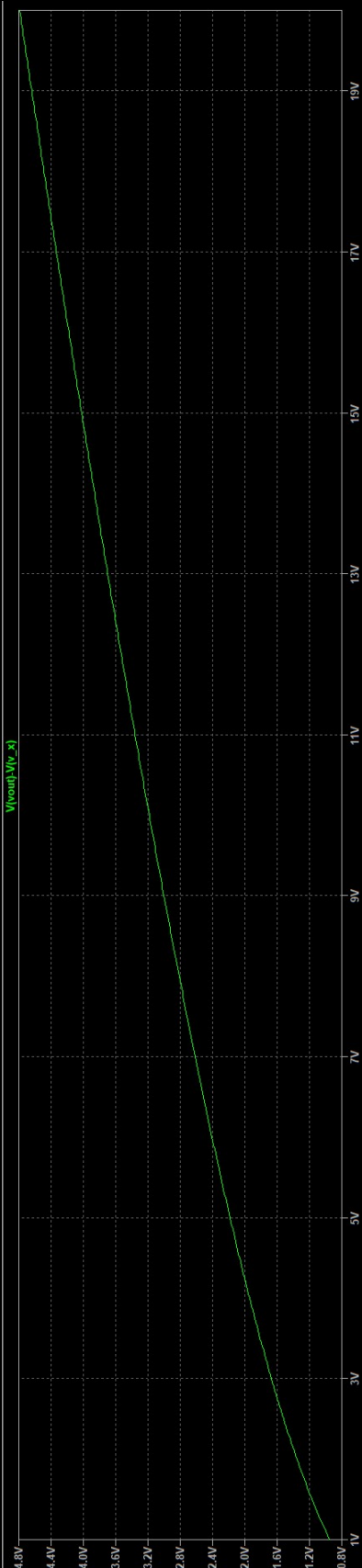


4 Circuit Schematics

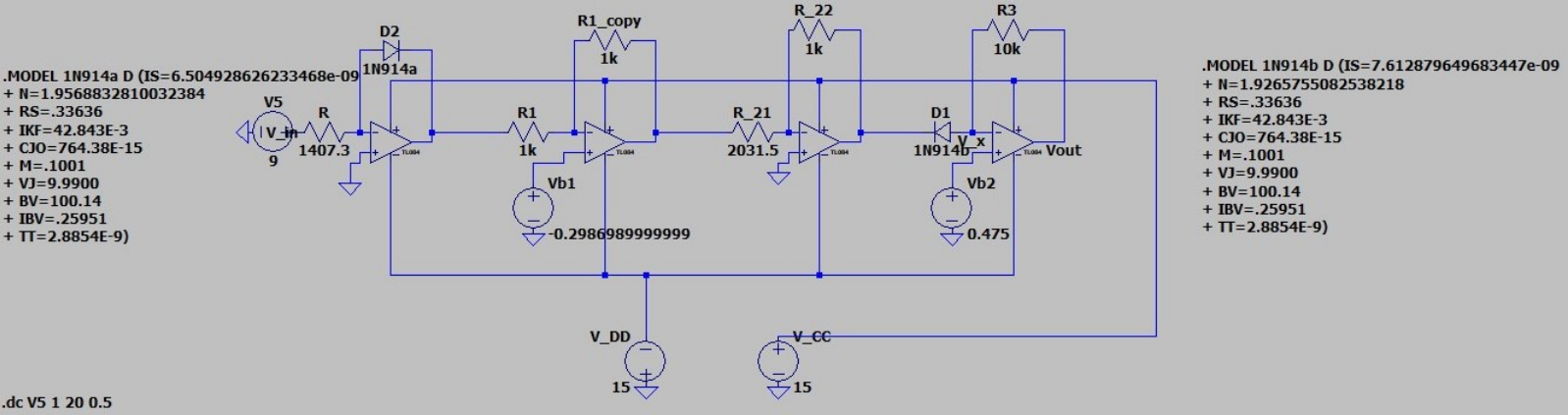


5 Experimental results


Plot $\ln(I_D)$ v/s V_D :

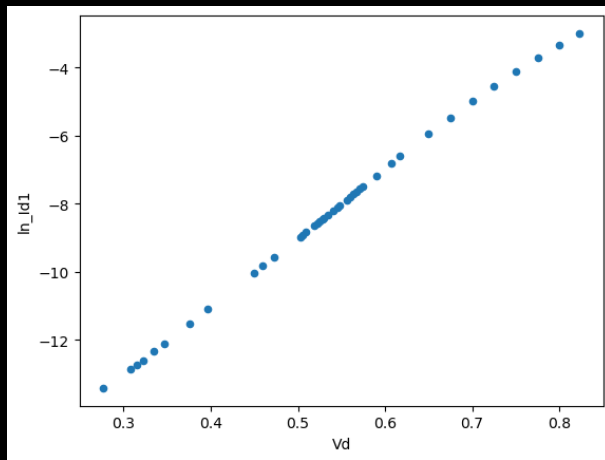


(a)

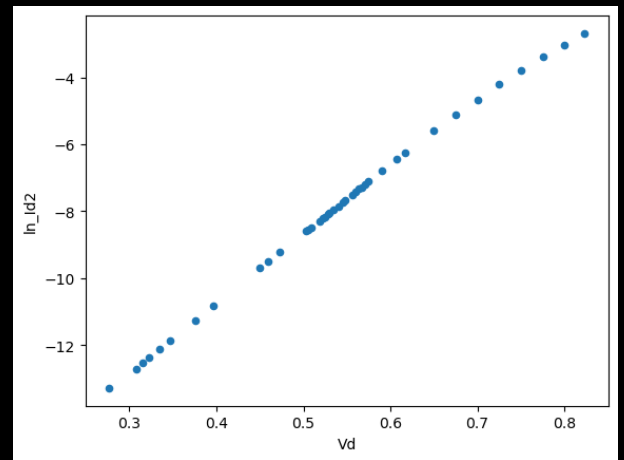


(b)

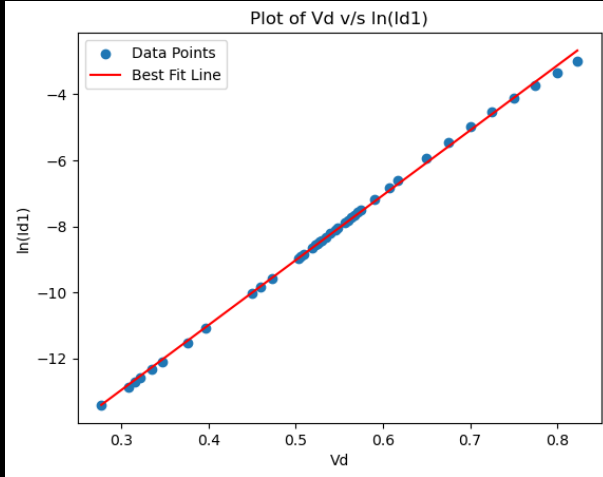

(a)

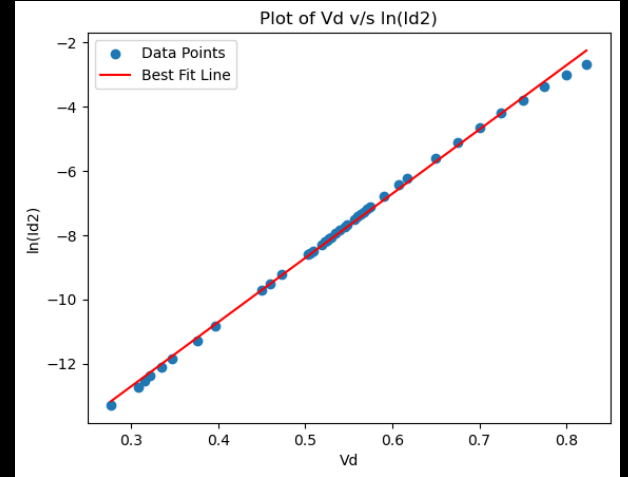

(b)

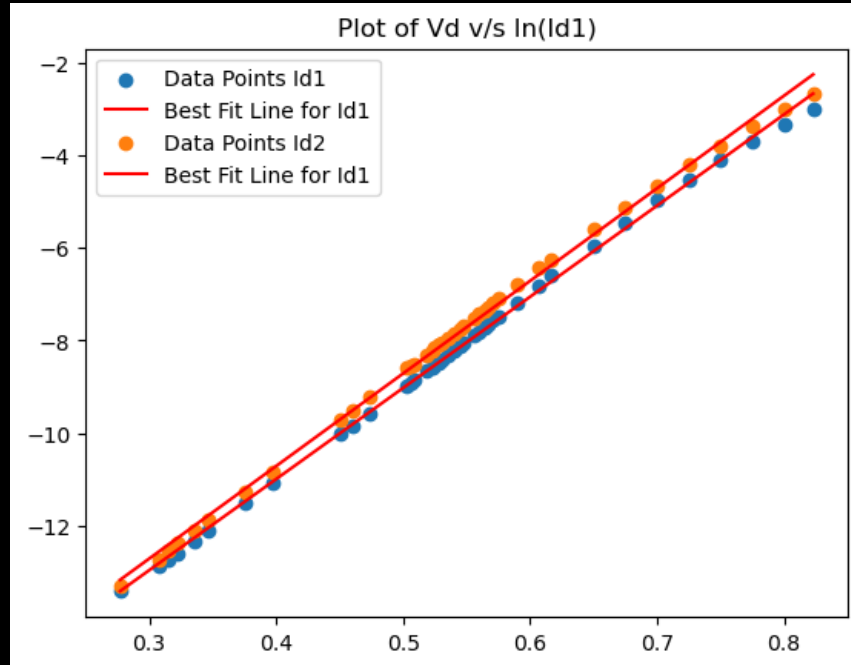

manually identify the range over which $\ln(I_D)$ is a linear function of V_D :

As it can be seen from the figure (a) on the top of this page, the last point to be on the line is, the values of which are - $V_D = 0.75$, $I_{D1} = 0.01633$ and

$$V_D = 0.725 \text{ and } I_{D2} = 1.48\text{e-}02$$

determine I_S and n :

The value of:

$$I_{S1} = \frac{1}{e^{18.8507}} = 6.5\text{e-}9$$

$$I_{S2} = \frac{1}{e^{18.6934}} = 7.6\text{e-}9$$

$$n_1 = \frac{1}{\text{slope}_1 \cdot V_T} = \frac{1}{19.65 \cdot 0.026} = 1.95$$

$$n_2 = \frac{1}{\text{slope}_2 \cdot V_T} = \frac{1}{19.96 \cdot 0.026} = 1.926$$

Choose diode for Block-1 and determine the value of R :

We'll choose Diode 1 since it's correlation is more i.e. it's linear over a larger range as compared to Diode 2. $I_{D1} = 0.01066$, $R = \frac{15}{I_{D1}} = \frac{15}{0.01066} = 1407.13\Omega$

Determine the expression for V_{out1} :

$$V_{out1} = n V_T (\ln(I_S R) - \ln(V_{in})) = 0.0508(-11.6 - \ln(V_{in}))$$

Determine V_{b1} to remove offset and choose R_1 arbitrarily:

$V_{b1} = \frac{nV_T \ln(I_S R)}{2} = -0.0294 \text{ V}$ and choosing $R_1 = 1\text{k}\Omega$. Corresponding V_{out1} becomes -0.589V .

Select V_{b2} and R_3 such that $V_{R3} = 1 \text{ V}$:

choosing $R_3 = 10\text{k}\Omega$

and substituting the values in equation (8) and equation (9), we get, $V_{R3} = 0.475$ for $R_3 = 10\text{k}\Omega$, $I_{S2} = 7.6\text{e-}09$, $n_2 = 19.96$ and $V_T = 0.026$.

Choose R_{21} and R_{22} and also fine tune for finding sqrt when $V_{in}=9\text{V}$:

We want $\beta_2 = \frac{1}{2}$ OR $\frac{n_1}{n_2} \cdot \frac{R_{22}}{R_{21}} = \frac{1}{2}$

$R_{21} = 2.03 * R_{22}$. Let's take $R_{22} = 1\text{k}\Omega$, $R_{21} = 2.03\text{k}\Omega$.

When we fine tune the circuit, we get, $V_{b1} = -0.2980989999999\text{V}$.

6 Experiment completion status

The full experiment along with the handwritten reports was completed during the lab hours.