

12/01/24

# EE230

## Lab-2



classmate

Date

Page


Ques 1

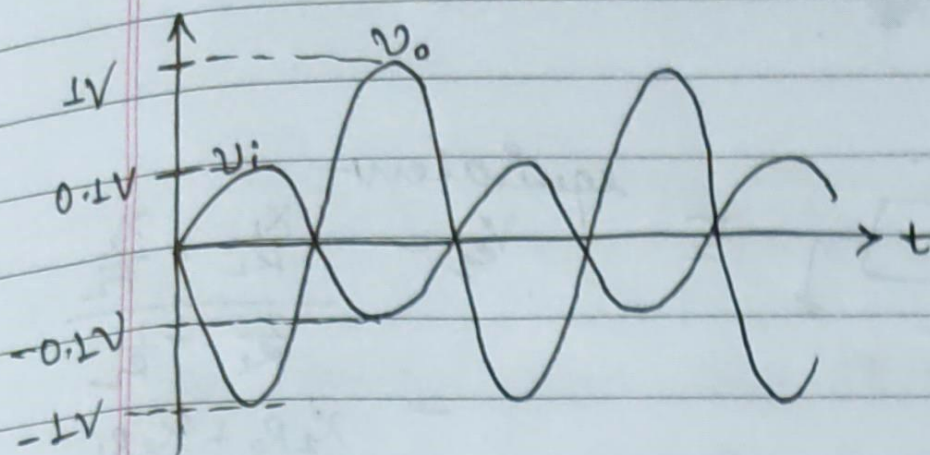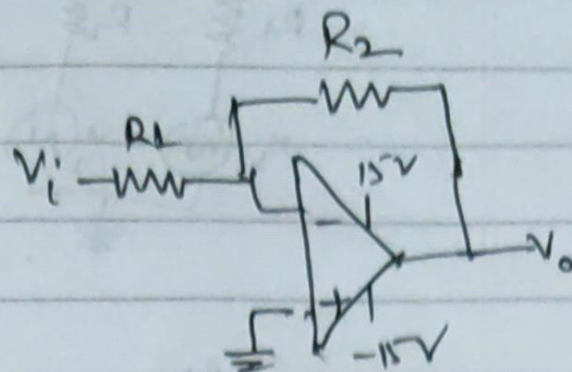- (a) i.  $R_1 = 1k\Omega$   
 $R_2 = 10k\Omega$





$V_o$  is phase shifted by  $180^\circ$  and scaled by 11 times ideally.  
 actual Gain = 10.

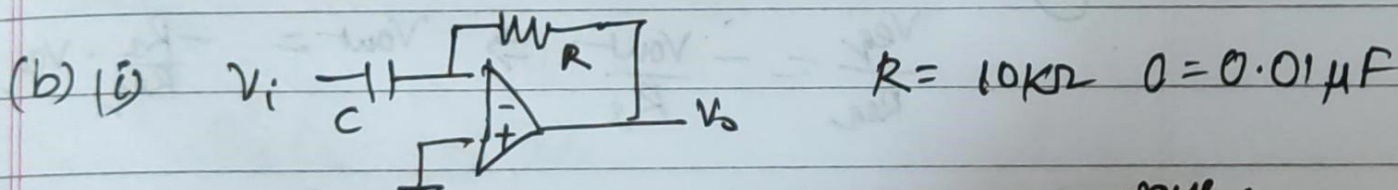(ii) As the voltage input increases, Volt. out. increases accordingly. But after reaching out to a input value of  $1.6V_{pp}$  the output starts clipping; beuz for  $1.6V_{pp}$  input; output should be  $16V$  but it's greater than the  $V_{DD}$  value of  $+15V$ , hence it gets clipped.



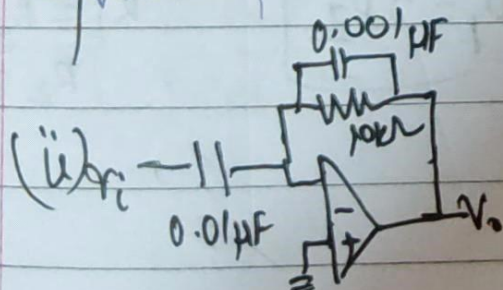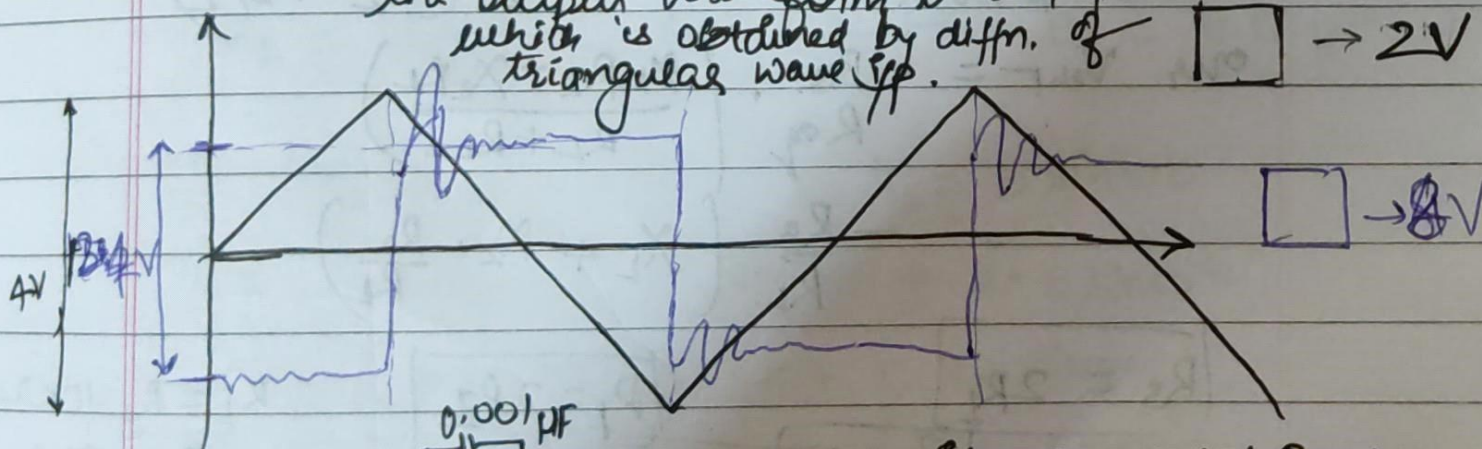The output waveform is a square wave; which is obtained by diffn. of triangular wave  $\uparrow$   $\rightarrow 2V$





The capacitor connected in parallel with the resistor stores the extra charge and hence dampens the noise effectively.

The pk to pk  $V_{out}$  comes down to  $5.8V$



(C)

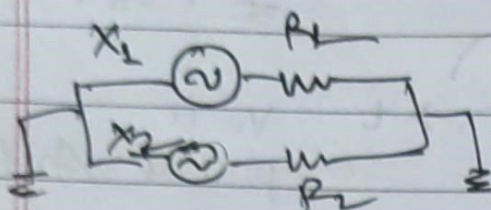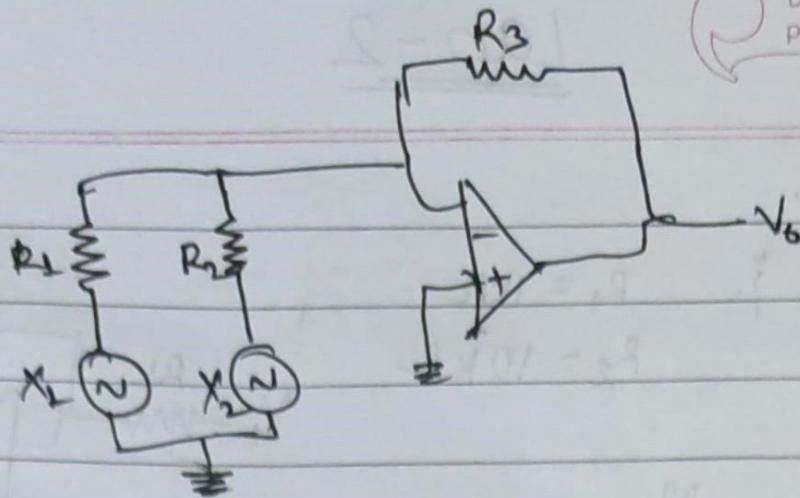


equivalent

$$V_{eq} = \frac{\frac{X_1}{R_1} + \frac{X_2}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}}$$

$$= \frac{X_1 R_2 + X_2 R_1}{R_1 + R_2}$$

equivalent
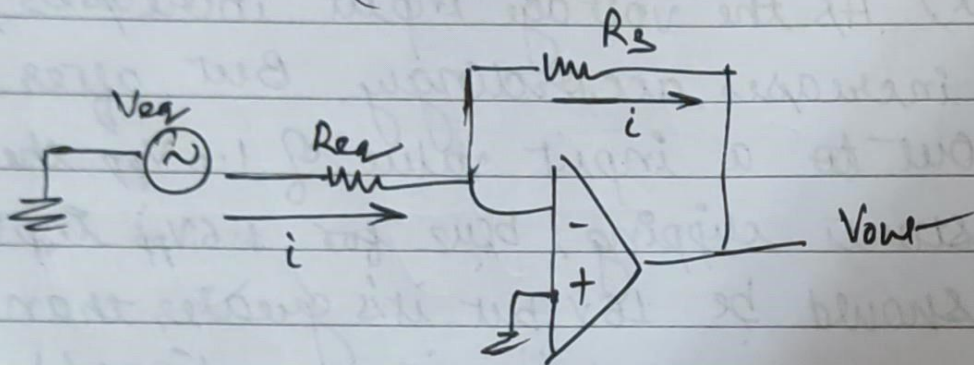
$$R_{eq} = \left( \frac{R_1 R_2}{R_1 + R_2} \right)$$



using Kirchhoff's law:

$$\frac{V_{eq}}{R_{eq}} = -\frac{V_{out}}{R_3} \Rightarrow V_{out} = -\frac{R_3}{R_{eq}} \cdot V_{eq}$$

$$V_{out} \text{ should be } = -2 \left( X_2 + X_1/2 \right)$$

$$\text{our } V_{out} = -\frac{R_3}{R_{eq}} \cdot \left( \frac{X_1 R_2 + X_2 R_1}{R_1 + R_2} \right)$$

$$= -\frac{R_3}{R_1} \left( X_1 + X_2 \cdot \frac{R_2}{R_1} \right)$$

$$R_3 = 2R_1$$


$$R_1 = R_2$$

$$R_3 = 2R_2$$

$$R_1 = R_3 = 10k\Omega$$

$$R_2 = 5k\Omega$$



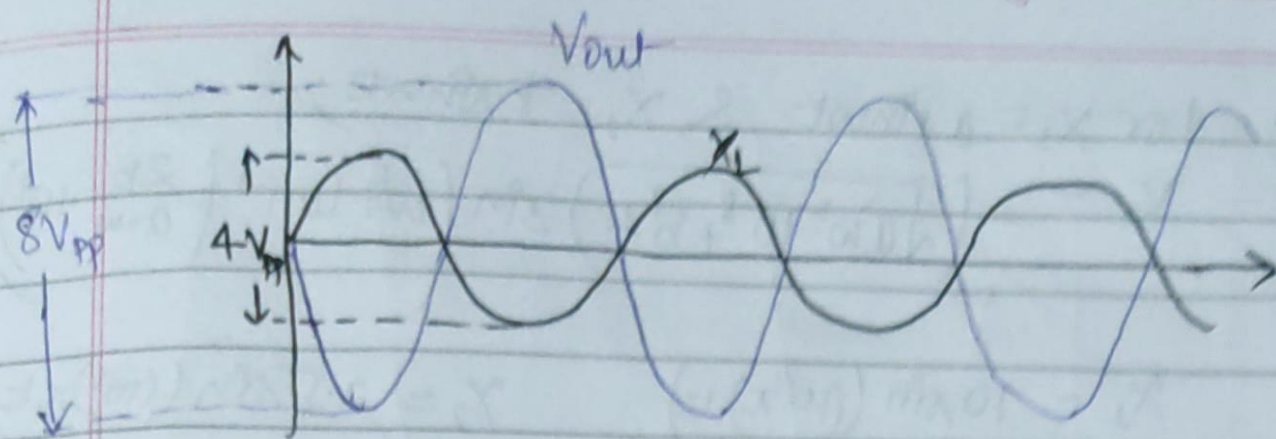

$$X_1 = 4V_{pp}$$

$$X_2 = 2V_{pp}$$

$$V_{out} = -2(2 + 4/2) = -8V_{out}$$


as expected from calculations the output voltage is twice of  $X_1$  and phase shifted by  $180^\circ$ .

(d) Equation solver:

$$(i) \quad V_o = - \left( 0.0001 \frac{d}{dt} X_1 + 2X_2 \right)$$

$$\frac{V_{out}}{X_2} = - \frac{R_2}{R_1} = - \frac{2}{1}$$

$$R_2 = 2R_1$$

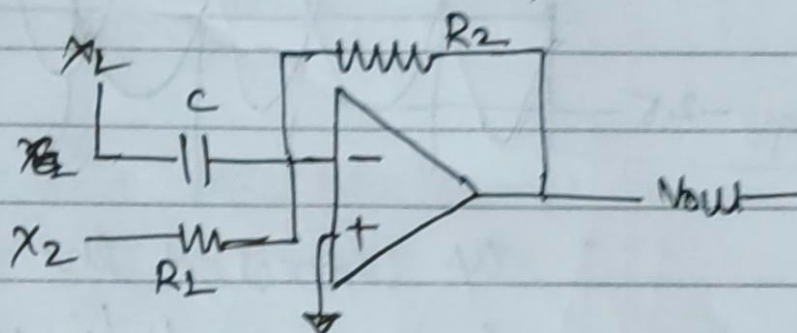

$$R_1 C_1 = 10^{-4} \text{ sec}$$

$$R_1 = 10K\Omega$$

$$R_2 = 20K\Omega$$

$$C_1 = 0.01\mu F$$

$$(ii) \quad X_1 = a \sin \omega t \quad X_2 = b \sin \omega t$$

$$V_o = - \left( 0.0001 \frac{d}{dt} (a \sin \omega t) + 2 \cdot b \sin \omega t \right)$$

$$= - \left( a \cdot \omega \cdot 10^{-4} \cos \omega t + 2b \sin \omega t \right)$$

$$= - \left( \sqrt{a^2 \omega^2 10^{-8} + 4b^2} \right) \sin \left( \omega t + \tan^{-1} \left( \frac{2b}{a \omega 10^{-4}} \right) \right)$$



(iii) for  $x_1 = a \sin \omega t$  &  $x_2 = b \sin \omega t$ ;

$$V_o = -(\sqrt{a^2 \omega^2 10^8 + b^2 4}) \sin\left(\omega t + \tan^{-1}\left(\frac{2b}{a \cdot \omega \cdot 10^4}\right)\right)$$

$$x_1 = 10 \sin(10^3 \pi t)$$


$$x_2 = 2.5 \sin((10^3)\pi t)$$

$$W = 10^2 \pi \quad a = 10 \quad b = 2.5$$

$$V_0 = - \left( \sqrt{\underbrace{10^8 \cdot 10^{-12}}_1 + \underbrace{4 \cdot 6.25}_{25}} \right) \sin \left( 10^3 \frac{t}{\mu\text{s}} + \tan^{-1} \left( \frac{5}{\cancel{10^4 \cdot 10^8}} \right) \right)$$


$$= \frac{1}{2} (\sqrt{26}) \sin(100 + 37) = 3.65$$
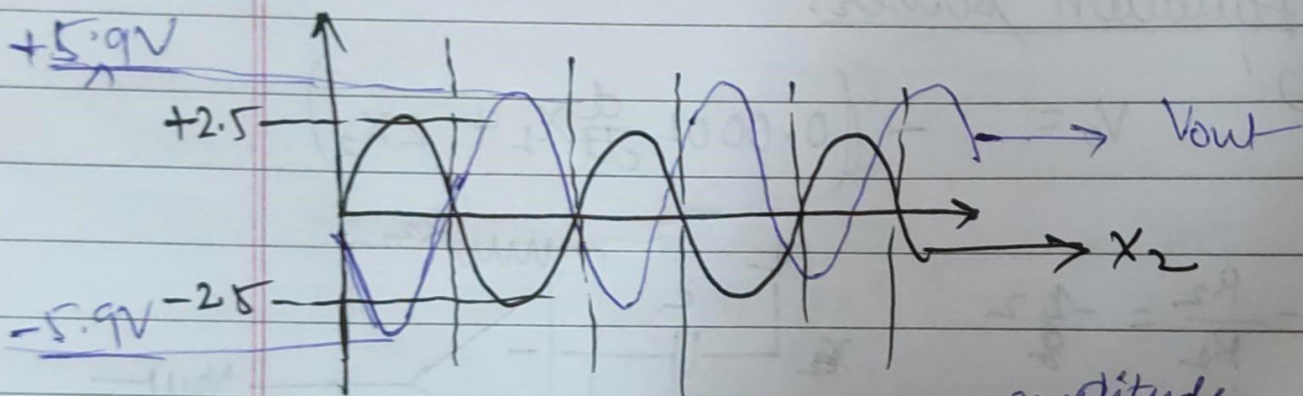
$$(b) = -5.9 \sin(2\pi \times 500t + 0.304)$$



As expected the output <sup>amplitude</sup> is 5.9 Volts and is inverted and further phase shifted by 0.3 radians

Ques 2 (a) Schmitt Trigger Ckt.

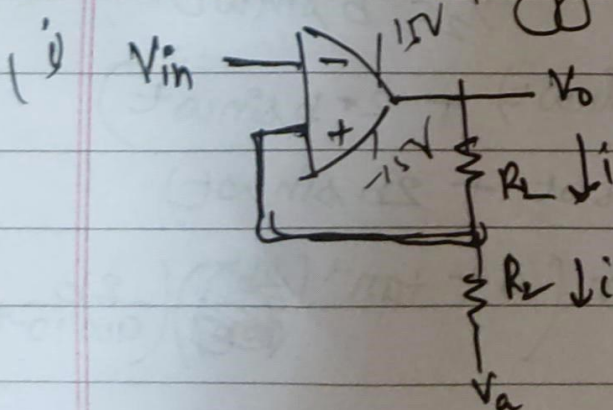

$$\frac{V_o - V_{in}}{R_2} = \frac{V_{in} - V_a}{R_2}$$

$$v_a = 0 \text{ (given)}$$

$$\frac{V_o - V_{in}}{R_1} = \frac{V_{in}}{R_2}$$

$$V_o = R_1 \left( V_{in} \left( \frac{1}{R_2} + \frac{1}{R_3} \right) \right)$$



$$V_{TH}(UTL) = 2.5V$$

$$V_{TH}(LTL) = -2.7V$$


$$V_o = V_{in} R_2 \left( \frac{1}{R_2} + \frac{1}{R_L} \right)$$

$$15V = (2.5V) \left( 1 + \frac{R_2}{R_1} \right)$$

$$5 = \frac{R_1}{R_2}$$

$$\underline{R_1 = 5R_2}$$
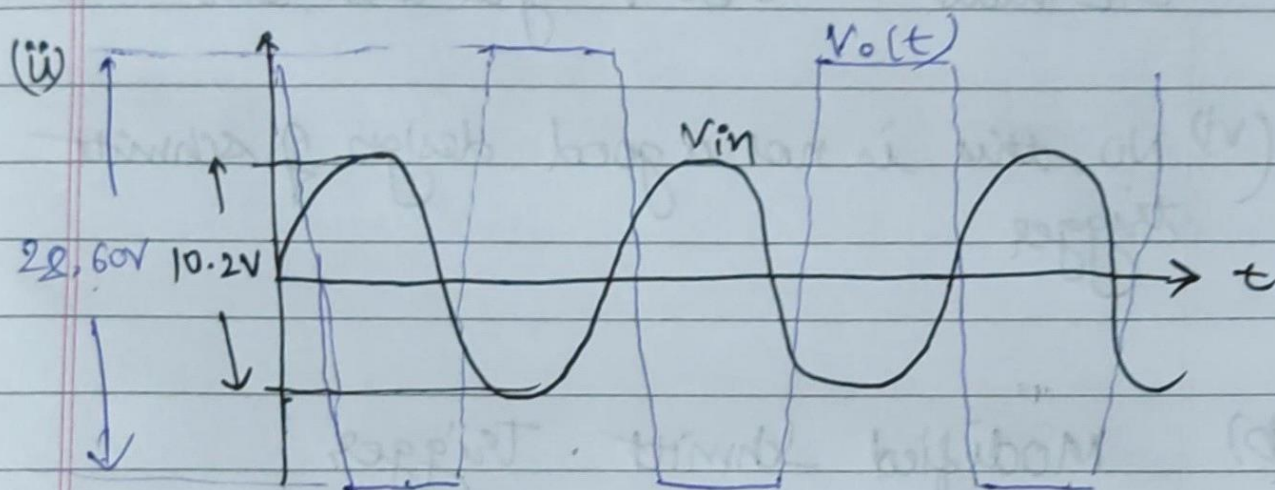
$$\underline{R_2 = 1k\Omega \quad R_L = 5k\Omega}$$



(iii) Observed threshold voltage comes out to be  $\pm 2.7V$ .


$$(iv) \quad \frac{V_o - V_{in}}{5k\Omega} = \frac{V_{in} - 2V}{1k\Omega} \Rightarrow V_o = 5 \left( V_{in} \left( 1 + \frac{1}{5} \right) - 2 \right)$$

$$\boxed{V_o = 6V_{in} - 10}$$

$$\begin{aligned} V_o &= 15V \\ 15V &= 6V_{in} - 10 \\ V_{in} &= \frac{25}{6}V \\ &= 4.166V \end{aligned}$$
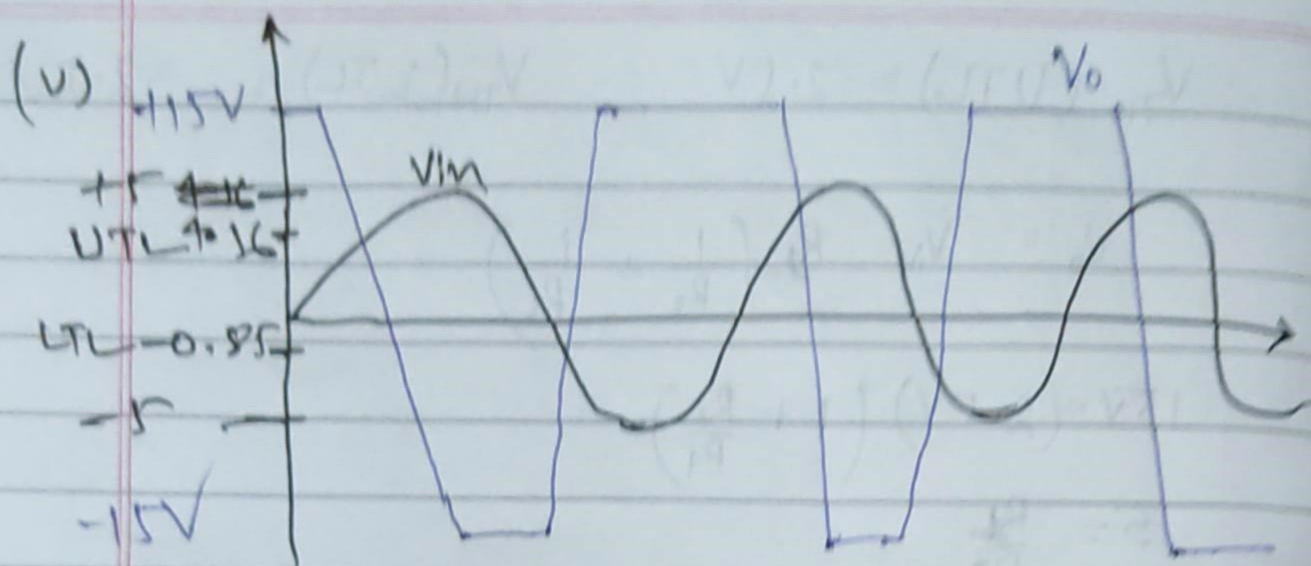
$$\begin{aligned} -15V &= 6V_{in} - 10 \\ V_{in} &= \frac{-5}{6}V \\ &= -0.85V \end{aligned}$$






the observed UTL value  $\rightarrow 4.16 \text{ V}$  &  
 LTL value  $\rightarrow -0.85 \text{ V}$  agree with our calculations

(vi) No, this is not a good design of Schmitt trigger

(b) Modified Schmitt Trigger

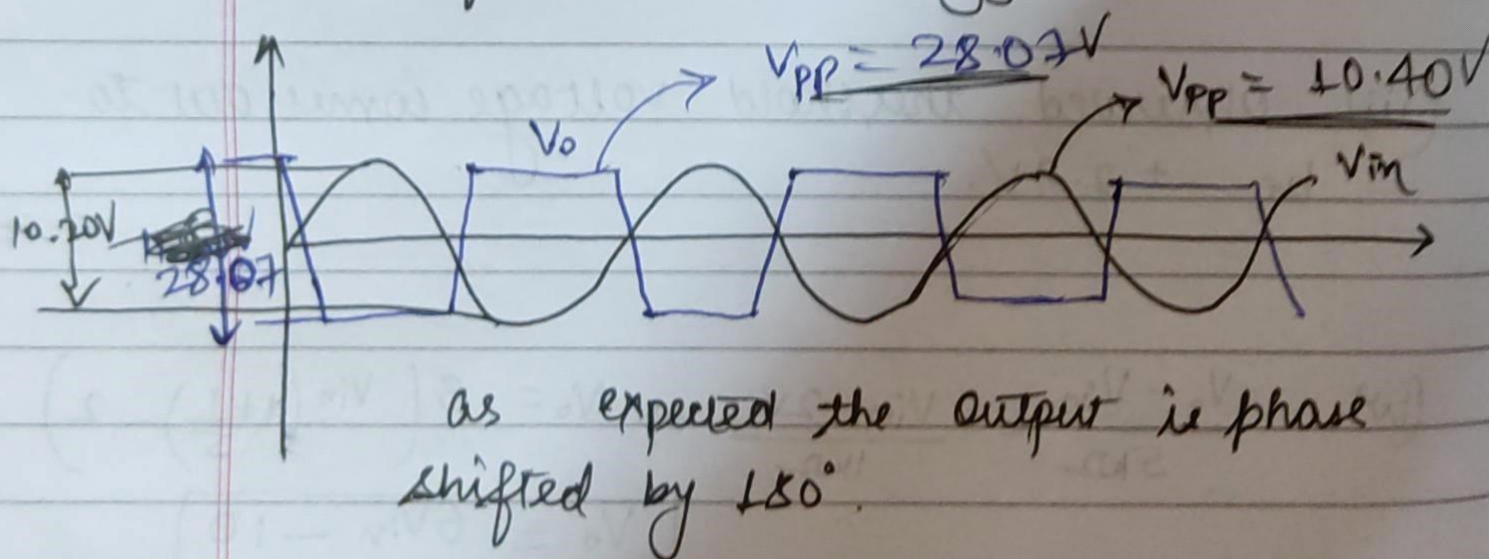

as expected the output is phase shifted by  $180^\circ$ .

observed  $V_{TH} = +3.2 \text{ V}$

$V_{TL} = -3 \text{ V}$

Gaurav  
 12/01/24